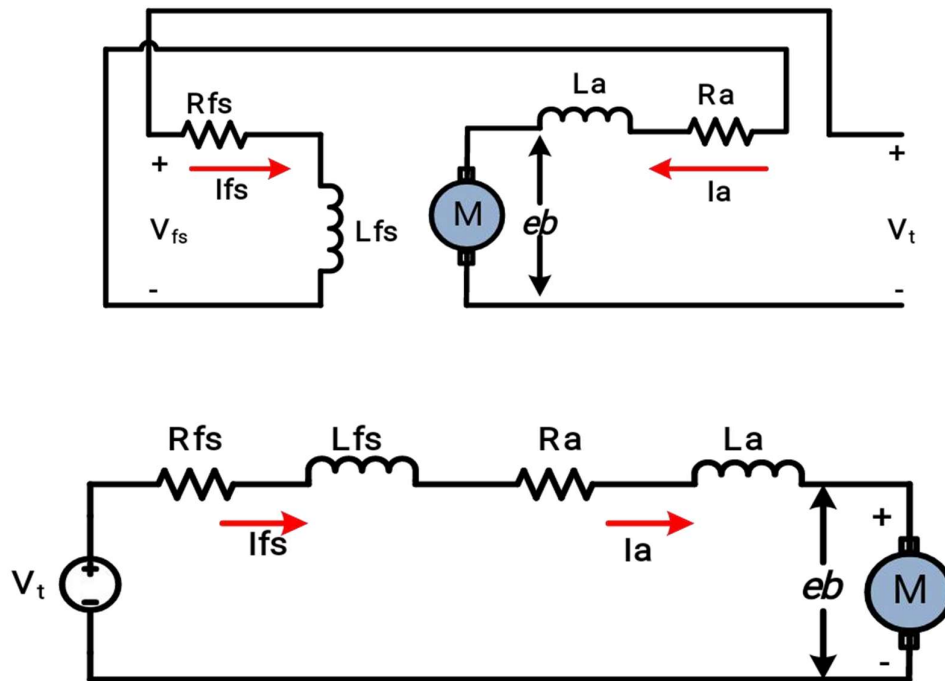


### Title of the Exercise: Series Excited DC motor

Date: 18.9.2020

**Aim:** To develop and Simulate mathematical dynamic model of DC Series motor and also

analyze with theoretical results. **Tool used:** MATLAB and SIMULINK Electrical Circuit:



$$T_e = L_{af} * I_f * I_a = L_{af} * I_a^2$$

### PARAMETERS USED FOR THE STUDY:

$R_a = 1.5$ ; Armature resistance in ohm

$L_a = 0.12$ ; Armature Inductance in Henry

$L_{fs} = 0.3$ ; Field Inductance in Henry

$R_{fs} = 0.7$ ; Field Resistance in ohms

$J = 0.02365$ ; Moment of Inertia

$B = 0.0025$ ; Friction Coefficient in

$L_{af} = 0.0675$ ; Mutual Inductance between field and armature Henry

$V_a = 240$ ; Supply DC voltage  $V_a = 240$  volts

**THEORETICAL ANALYSIS:**

In the motor mode, the field and armature of a dc series motor are supplied with the same current by an applied voltage, and a magnetic field (flux) is produced in the magnetic circuit.

**CALCULATIONS (PREDETERMINATION):**

Applying Kirchoff's Voltage Law:

$$V_t = I_{fs} + R_{fs} + L_{fs} * dI_{fs}/dt + I_a R_a + L_a * dI_a/dt + e_b$$

Value of back emf ( $e_b$ ) is given by

$$E_b = I_f * L_{af} * w$$

But in series excited DC Motor,  $I_{fs} = I_{fa} + I_a$

$$E_b = I_a * L_a * w$$

Electromagnetic torque equation is given by:

$$T_e = L_{af} * I_f * I_a$$

$$T_e = L_{af} * (I_a)^2$$

According to torque equation ,

$$T_e = T_l + j(dw/dt) + B * w$$

In steady state,

$$dI_a/dt = 0 ; dw/dt = 0$$

Therefore,

$$V_t = I_a (R_{fs} + R_a)$$

$$e_b = L_{af} * I_a$$

$$T_e = L_{af} * (I_a)^2$$

$$T_e = T_l + B * w$$

On substituting the input values to the above equations, we get:

$$1.8225 (I_a)^2 - 537.2 I_a - 240 = 0$$

$$I_a = 17.397 \text{ A}$$

Substituting this value in equation

$$2.2 * I_a = 240 - L_{af} * I_a * w$$

$$w = 171.724 \text{ rad/s}$$

From the torque equation, we get


$$T_e = 20.429 \text{ Nm}$$

From the back emf (eb) equation, we get

$$e_b = 201.644 \text{ V}$$

### **PROCEDURE FOR SIMULATION STUDY:**

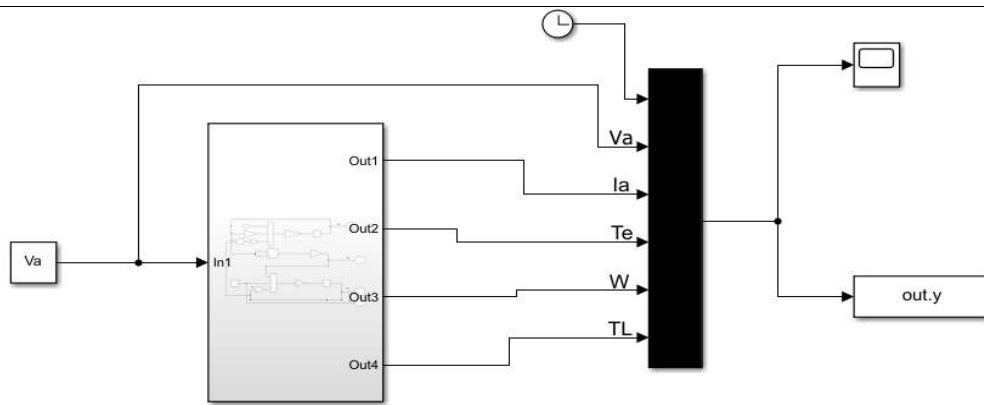1. Write the coding for Initialize the input parameters and as per the requirement of plots in m file and save it.
2. Open new Simulink file and make mathematical modelling as per circuit diagram and save it.
3. Run the m file first, after that run Simulink file.
4. View the result in Scope.
5. Again run m file and view the plots.
6. Make various plots and write the Results.



### Mfile code:



```

Ra=1.5;
Ia = 0.12;
Lf= 0.3;
Rf= 0.7;
J= 0.02365;
B= 0.0025;
Laf = 0.0675;
Va= 240;
keyboard
subplot(5,1,1)
plot(out.y.signals.values(:,1),out.y.signals.values(:,2),'b-')
title('Armature Voltage')
ylabel('Va In volts')
subplot(5,1,2)
plot(out.y.signals.values(:,1),out.y.signals.values(:,5),'g--.')
title('Speed')
ylabel('Wr in rad/sec')
subplot(5,1,3)
plot(out.y.signals.values(:,1),out.y.signals.values(:,6),'y--.')
title('Load Torque')
ylabel('TL in N/m')
subplot(5,1,4)
plot(out.y.signals.values(:,1),out.y.signals.values(:,3),'k--.')
title('Armature Current')
ylabel('Ia in Amp')
subplot(5,1,5)
plot(out.y.signals.values(:,1),out.y.signals.values(:,4),'c--.')
title('Electromagnetic Torque')
ylabel('Te in N/m')
xlabel('Time in sec')

```

### STIMULATION AND M.FILE CODING:

## RESULTS AND DISCUSSIONS:

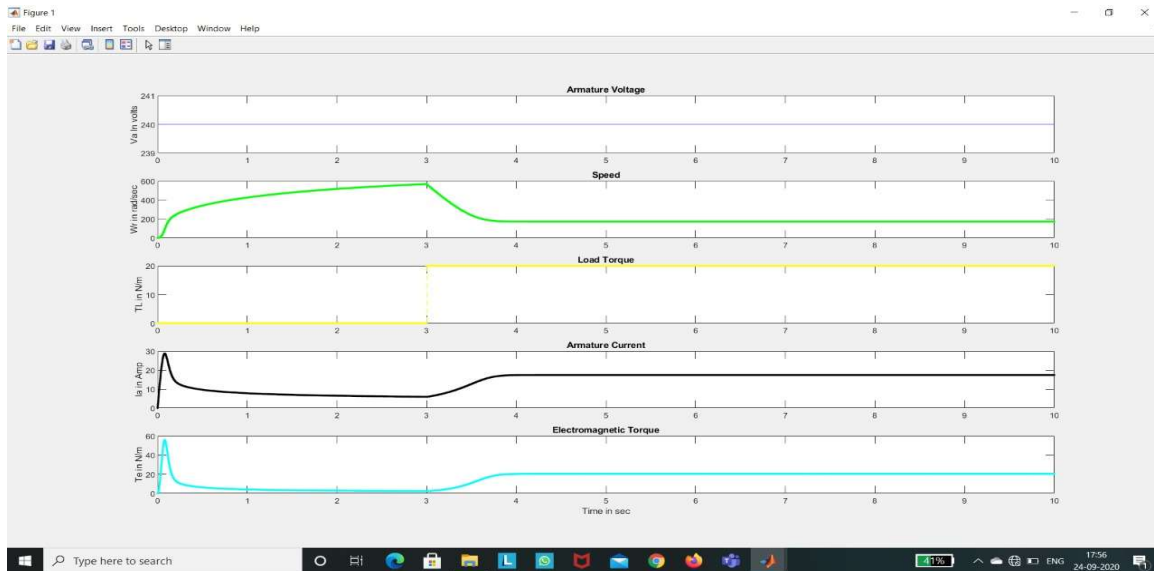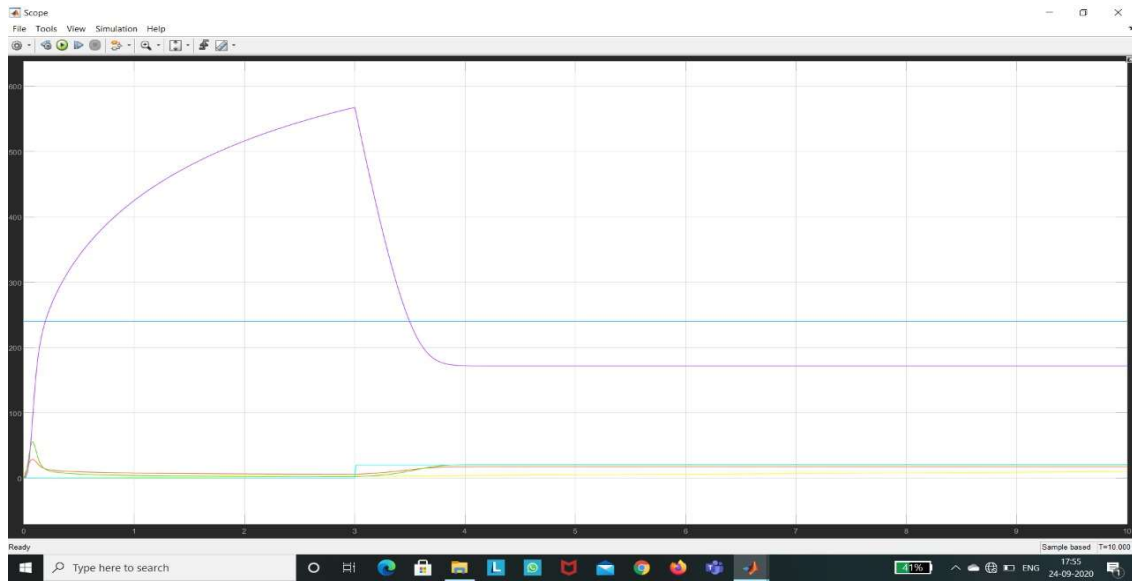

**Comparison (Observations)**

Time	Theoretical (current)	Simulation (current)
6.301	17.42	17.41

Time	Theoretical (electromagnetic torque)	Simulation (electromagnetic torque)
6.893	20.41	20.41

Time	Theoretical (speed)	Simulation (speed)
8.483	171.7	171.7

**Conclusion : The theoretical and experimental values match.**

**Inference :**

In this motor, field, as well as stator windings, are coupled in series by each other. Accordingly the armature and field current are equivalent. When voltage is applied, current flows from power supply terminals through the series winding and armature winding.

**References**