


Title of the Assignment: SHORT SHUNT DC COMPOUND MOTOR

Date: 18/09/2020

Aim: To develop and simulate mathematical dynamic modal of a Short Shunt DC Compound Motor and also analyze its theoretical results.

Tool used: MATLAB and Simulink

Electrical Circuit:

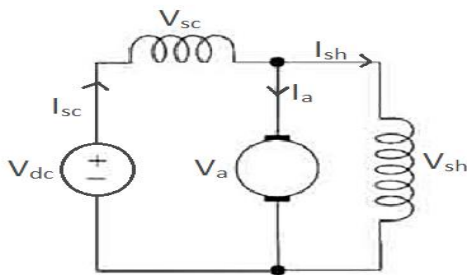

Parameters used for the study:

Input voltage, $V_{dc} = 230$ V
Armature resistance, $R_a = 1.50$ ohms
Armature winding self-inductance, $L_a = 0.12$ H
Mutual inductance between armature and main field, $L_{ash} = 1.8$ H
Mutual inductance between armature and series field, $L_{ase} = 0.0018$ H
Shunt field winding resistance, $R_{sh} = 270$ ohm
Shunt field winding self-inductance, $L_{sh} = 0.03$ H
Mutual inductance between series and shunt field, $L_{shse} = 0.001$ H
Self-inductance of series field winding, $L_{se} = 0.012$ H
Series armature winding resistance, $R_{se} = 0.7$ ohms
Back emf constant or torque constant, $K = 0.0141$
Moment of inertia, $J = 0.02365$
Friction coefficient, $B = 0.0025$
Rated load = 2.5HP

Theoretical Analysis:

$$\begin{aligned}V_a &= I_a \cdot R_a + L_a \cdot (dI_a / dt) + E_b \\V_{sh} &= I_{sh} \cdot R_{sh} + L_{sh} \cdot (dI_{sh} / dt) + L_{shsc} \cdot (dI_{sc} / dt) \\V_{sc} &= I_{sc} \cdot R_{sc} + L_{sc} \cdot (dI_{sc} / dt) + L_{shsc} \cdot (dI_{sh} / dt) \\E_b &= L_{ash} \cdot \omega \cdot I_{sc} + L_{ash} \cdot \omega \cdot I_{sh} \\T_e &= L_{ash} \cdot I_a \cdot I_{sc} + L_{ash} \cdot \omega \cdot I_{sh} \\T_e &= T_l + B \cdot \omega + j(d\omega / dt) \\V_{dc} &= V_a + V_{sc} = V_{se} + V_{sh} \\V_a &= V_{sh}\end{aligned}$$

Calculations (Predetermination)

At steady state:

$$dI_a/dt = 0, dI_{sc}/dt = 0, dI_{sh} = 0,$$

$$V_a = I_a R_a + E_b$$

$$V_{sh} = I_{sh} R_{sh}$$

$$V_{sc} = I_{sc} R_{sc}$$

$$V_a = 1.5 I_a + E_b$$

$$T_e = 10 + B \cdot \omega$$

$$V_{sh} = 270 I_{sh}$$

$$V_{sc} = 0.7 I_{sc}$$

$$T_e = 10 + 0.0025 \omega$$

$$T_e = 1.8 I_a (I_{sc} + I_{sh})$$

$$E_b = 1.8 \omega (I_{sc} + I_{sh})$$

On solving we the above equations we get

$$E_b = 220.34 \text{ V}$$

$$\omega = 36.443 \text{ rad/s}$$

$$I_{sc} = 2.515 \text{ A}$$

$$I_a = 1.67 \text{ A}$$


$$I_{sh} = 0.845 \text{ A}$$

$$T_e = 10.09$$

Procedure for simulation study:

- Write the coding for initializing the input parameters and as per requirement of plots in m file and save it.
- Open new Simulink file and make mathematical modelling as per circuit diagram and save it.
- Run the m file first, after that run Simulink file.
- View the result in Scope.
- Again, run m file and view the plots.
- Make various plots and write the results.

Simulink model and m file

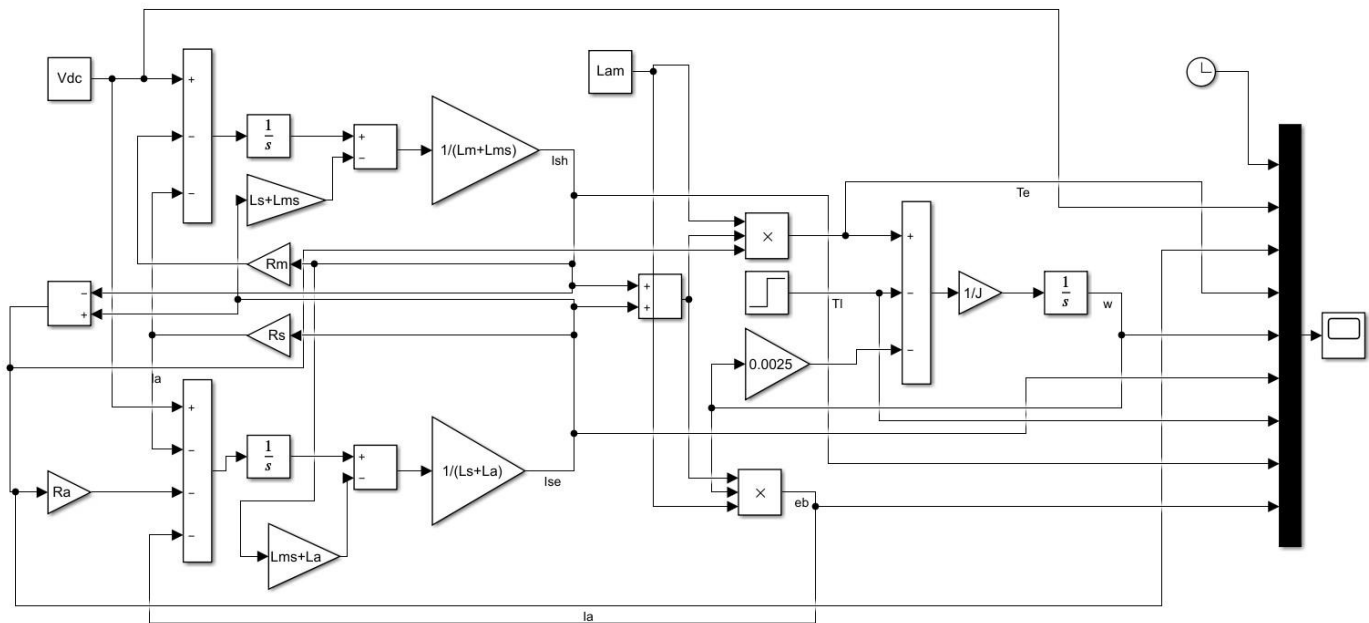

m file:

```

Vdc = 230;
Ra = 1.50;
Rm = 270;
Rs = 0.7;
La = 0.12;
Lam = 1.8;
Las = 0.0018;
Lm = 0.03;
Lms = 0.001;
Ls = 0.012;
J = 0.02365;
K = 0.0141;
subplot(6,1,1)
plot(out.y(:,1),out.y(:,2))
title('Input Voltage')
ylabel('Vdc in Volts')
subplot(6,1,2)
plot(out.y(:,1),out.y(:,4))
title('Electromagnetic Torque')
ylabel('Te in N/m')
subplot(6,1,3)
plot(out.y(:,1),out.y(:,8))
title('Main Winding Current')

```


```

plot(out.y(:,1),out.y(:,3))
title('Armature Current')
ylabel('Ia in A')
subplot(6,1,5)
plot(out.y(:,1),out.y(:,5))
title('Speed')
ylabel('Wr in rad/sec')
subplot(6,1,6)
plot(out.y(:,1),out.y(:,7))
title(' Load Torque')
ylabel('TL in N/m')


```

Results and Discussions

Graph from M file

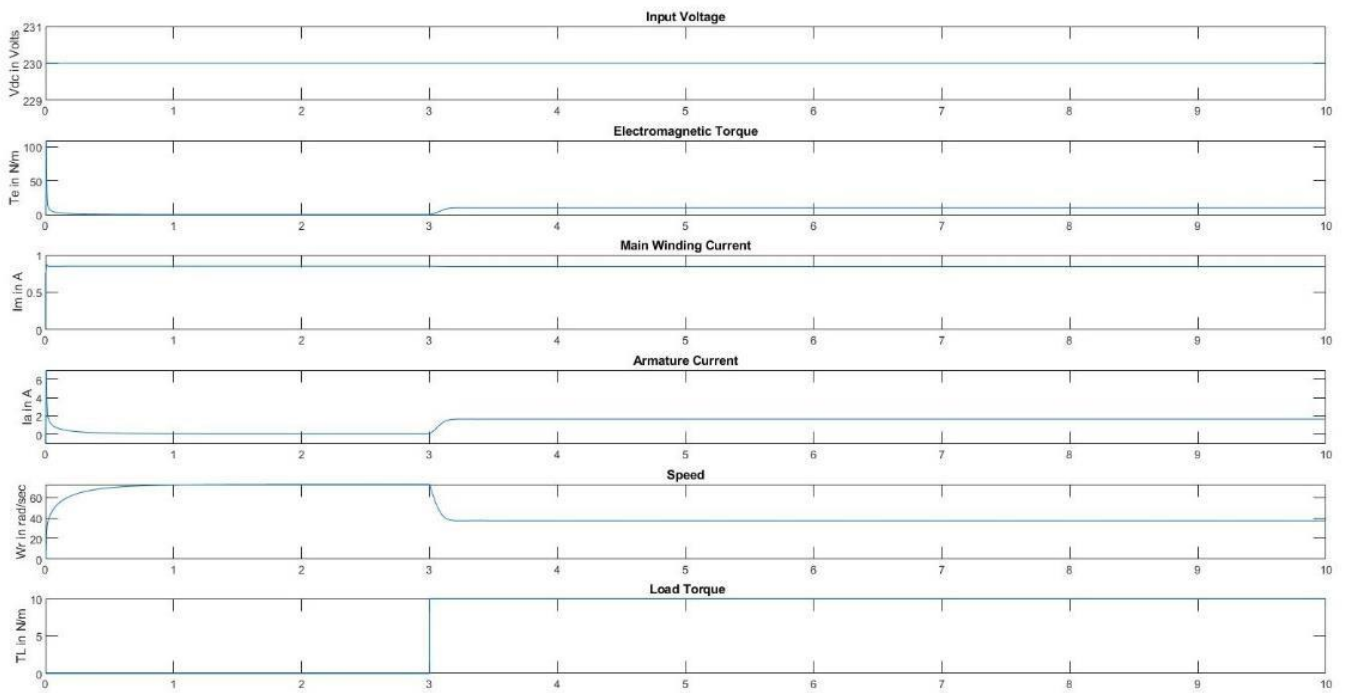

Scope output graph

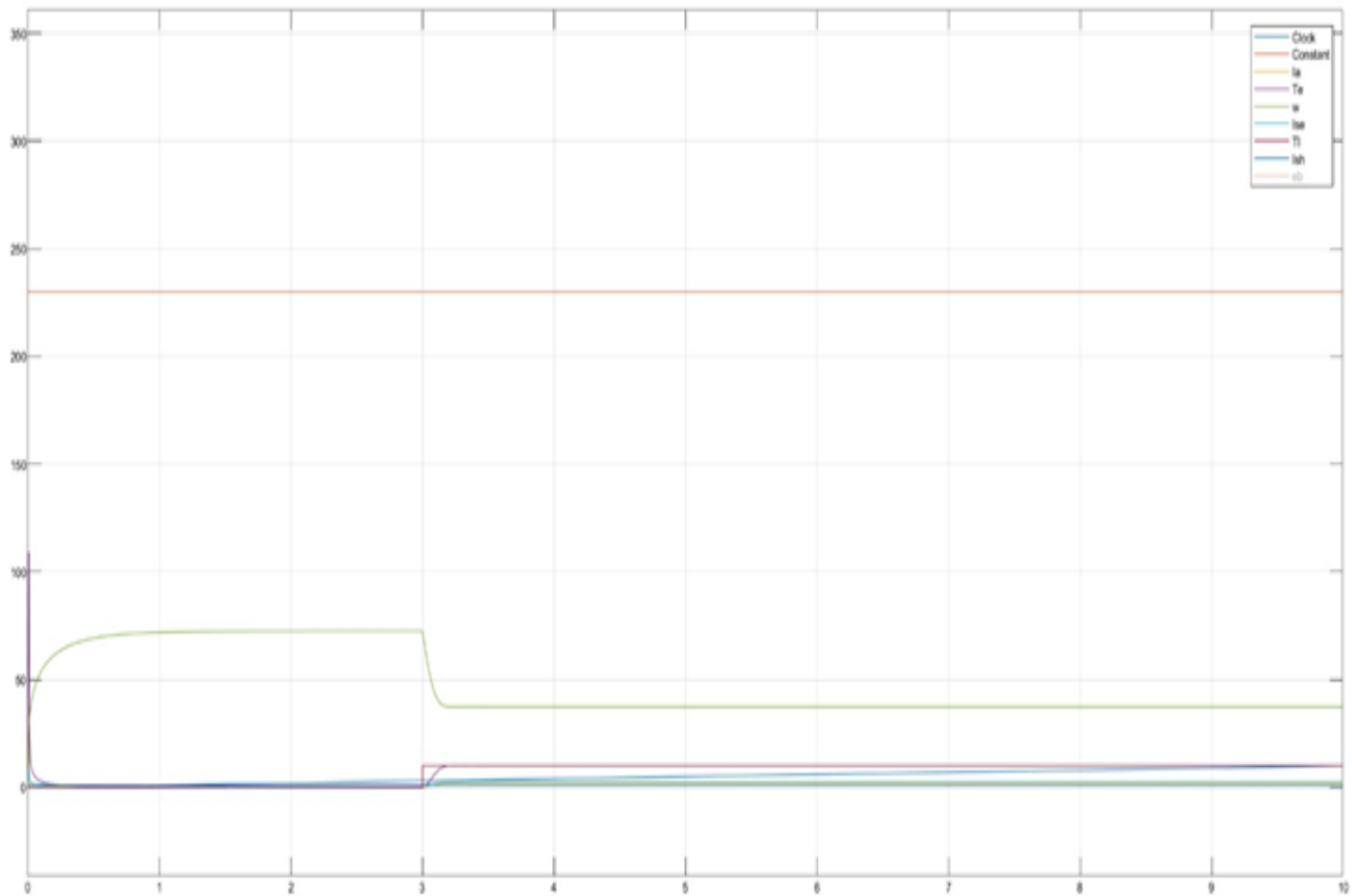

Parameter	Value
I_a	1.67 A
T_e	10.09
ω	36.443 rad/s
I_{se}	2.515 A
E_b	220.34 V
I_{sh}	0.845 A

Comparison (Observations):

Parameter	Theoretical Value	Simulation Value
I_a	1.67 A	1.669 A
T_e	10.09	10.091
ω	36.443 rad/s	37.33 rad/s
I_{se}	2.515 A	2.514 A
E_b	220.34 V	225.5 V
I_{sh}	0.845 A	0.845 A

Conclusion: Hence the simulation values match with the theoretical values and a dynamic model of a DC short Shunt Motor has been successfully simulated.

Inference: Therefore, characteristic graphs of elements in the circuit are obtained and verified against theoretical values in steady state.

References:

- Simulink Onramp
- MATLAB onramp