

Title of the Exercise: Exercise 6 : Long shunt DC motor

Date: 18/09/2020



Aim

To Simulate the dynamic modal of a long shunt DC motor plot various characteristics curves and analyse the results.

Tool used :

MATLAB

Electrical Circuit

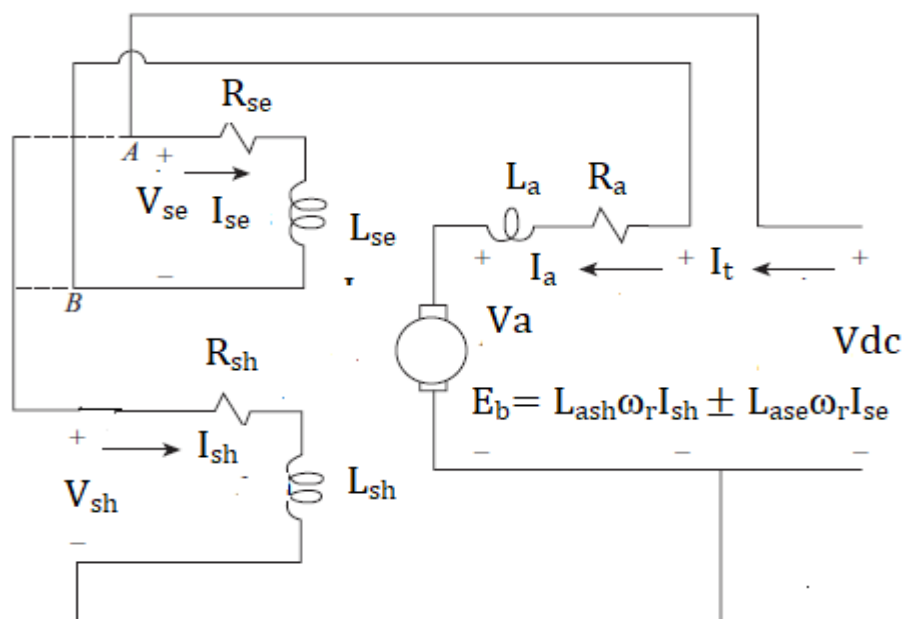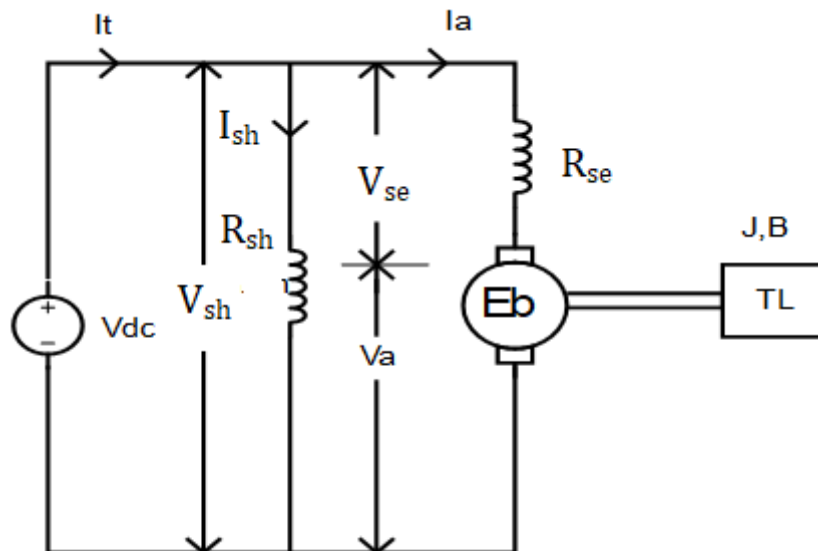

Parameters Used for study:

Input voltage $V_{dc}=230$,

Armature resistance $R_a = 1.50$ ohms

Armature winding self inductance $L_a=0.12H$

Mutual inductance between armature and main field $L_{ash}=1.8H$

Mutual inductance between armature and series field $L_{ase}=0.0018H$

Shunt field winding resistance $R_{sh}=270$ ohm

Shunt field winding Self inductance $L_{sh}=0.03H$

Mutual inductance between series and Shunt field $L_{shse}= 0.001H$

Self inductance of series field winding $L_{se}=0.012 H$

Series armature winding resistance $R_{se}=0.7ohms$

Back emf constant or torque constant $K=0.0141$

Moment of inertia $J=0.02365$

Friction coefficient $B=0.0025$

Rated load=2.5HP

Theoretical Analysis

$$V_{dc}=V_{sh}$$

$$V_{dc}=V_a+V_{se}$$

$$I_t= I_{sh}+I_{se}$$

$$I_{se}=I_a$$

$$V_{dc}=I_{sh} R_{sh}$$

$$V_{dc}=V_{se}+V_a=I_a(R_{se}+R_a)+E_b$$

$$V_{sh}=R_{sh} I_{sh} + L_{sh} \frac{dI_{sh}}{dt} \pm L_{shse} \frac{dI_{se}}{dt}$$

$$V_{se}=R_{se}I_{se}+ L_{se} \frac{dI_{se}}{dt} \pm L_{shse} \frac{dI_{sh}}{dt}$$

$$V_a=R_a I_a+ L_a \frac{dI_a}{dt}+ L_{ash} \omega_r I_{sh} \pm L_{ase} \omega_r I_{se}$$

$$E_b= L_{ash} \omega_r I_{sh} \pm L_{ase} \omega_r I_{se}$$

$$T_e=L_{ash} I_{se} I_{sh} \pm L_{ase} I_{se} I_a$$

$$T_e=T_L + J \frac{d\omega}{dt} + B\omega$$

Calculations (Predetermination):

In steady state:

$$dI_a/dt = 0$$

$$dI_{sh}/dt = 0$$

$$d\omega/dt = 0$$

then we get

$$V_{sh} = R_{sh} I_{sh}$$

$$V_{se} = R_{se} I_{se} = R_{se} I_a$$

$$V_a = R_a I_a + E_b$$

$$V_b = L_{ash} W_r I_{sh} + L_{ase} W_r I_{se}$$

$$= L_{ash} W_r I_{sh} + L_{ase} W_r I_a$$

$$T_e = L_{ash} I_{sh} I_a + L_{ase} I_a^2$$

$$T_e = T_l + B W_r$$

Substituting the values

$$V_{dc}=230$$

$$R_a = 1.50 \text{ ohms}$$

$$L_a=0.12H$$

$$L_{ash}=1.8H$$

$$L_{ase}=0.0018H$$

$$R_{sh}=270 \text{ ohm}$$

$$L_{sh}=0.03H$$

$$L_{shse}= 0.001H$$

$$L_{se}=0.012 \text{ H}$$

$$R_{se}=0.7\text{ohms}$$

$$K=0.0141$$

$$J=0.02365$$

$$B=0.0025$$

We get

$$I_{sh} = V_{sh}/R_{sh} = 230/270 = 0.851A$$

$$V_a = 230 - 0.7I_a$$

-----Eqn 1

$$V_a = 1.5I_a + 1.8*0.852W_r + 0.0018W_r I_a$$

-----Eqn 2

$$T_e = 10 + 0.0025W_r$$

-----Eqn 3

$$T_e = 1.8*0.852I_a + 1.8T_a^2$$

-----Eqn 4

On solving the equations we get

$$I_a = 1.99A$$

$$T_e = 10.11Nm$$


$$W_r = 44.22rad/sec$$

$$E_b = 67.89V$$

Procedure for simulation study:

- 1)Write down the mathematical equations according to the circuit diagram
- 2)Make the m file and initialise all the the constants in it
- 3)Open a blank Simulink model and make the Simulink model according to the equations
- 4)save the Simulink file and run it
- 4)Note the readings from the scope

Simulation Diagram and m.file coding

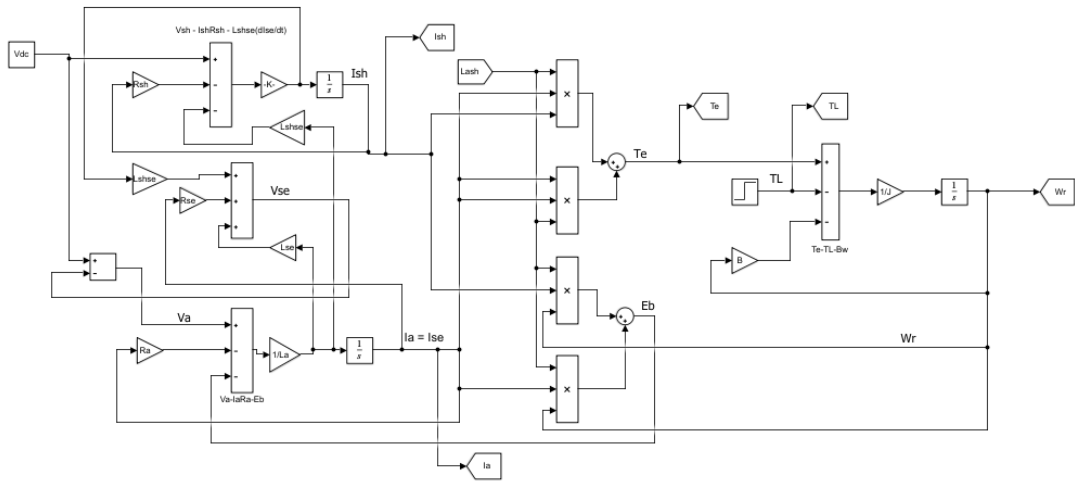

```

Vdc=230;
Ra=1.50;
La=0.12;
Lash=1.8;
Lase=0.0018;
Rsh=270;
Lsh=0.03;
Lms=0.0018;
Lshse=0.001;
Lse=0.012;
Rse=0.7;
K=0.0141;
J=0.02365;
B=0.0025;
disp('run simulation,type "return" when ready to return')
keyboard
subplot(6,1,1)
plot(out.y(:,1),out.y(:,2))
title('Armature voltage')
ylabel('Va in Volts')
subplot(6,1,2)
plot(out.y(:,1),out.y(:,3))
title('Armature Current')
ylabel('Ia in A')
subplot(6,1,3)
plot(out.y(:,1),out.y(:,4))
title('Electromagnetic torque')
ylabel('Te in N/m')
subplot(6,1,4)
plot(out.y(:,1),out.y(:,5))
title('Speed')
ylabel('w in m/s')
subplot(6,1,5)
plot(out.y(:,1),out.y(:,6))
title('Winding current')
ylabel('Ish in A')
subplot(6,1,6)



```

```

plot(out.y(:,1),out.y(:,7))
title('Load torque')
ylabel('Tl in N/m')
xlabel('time in s')

```

Results and Discussions:

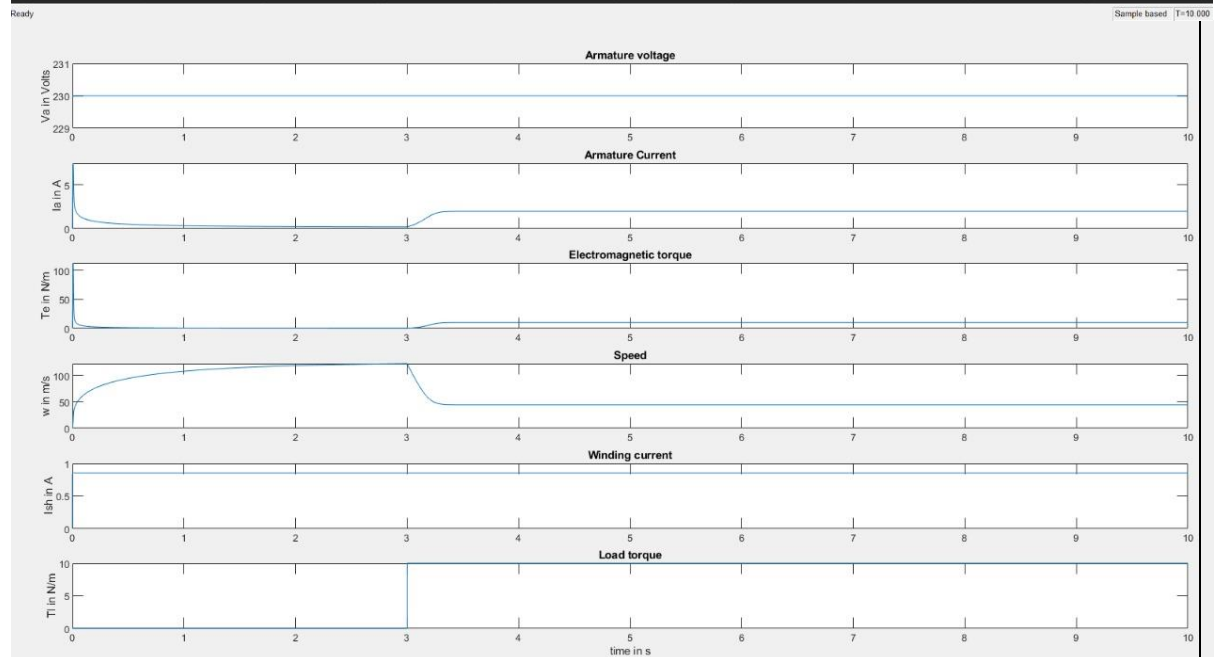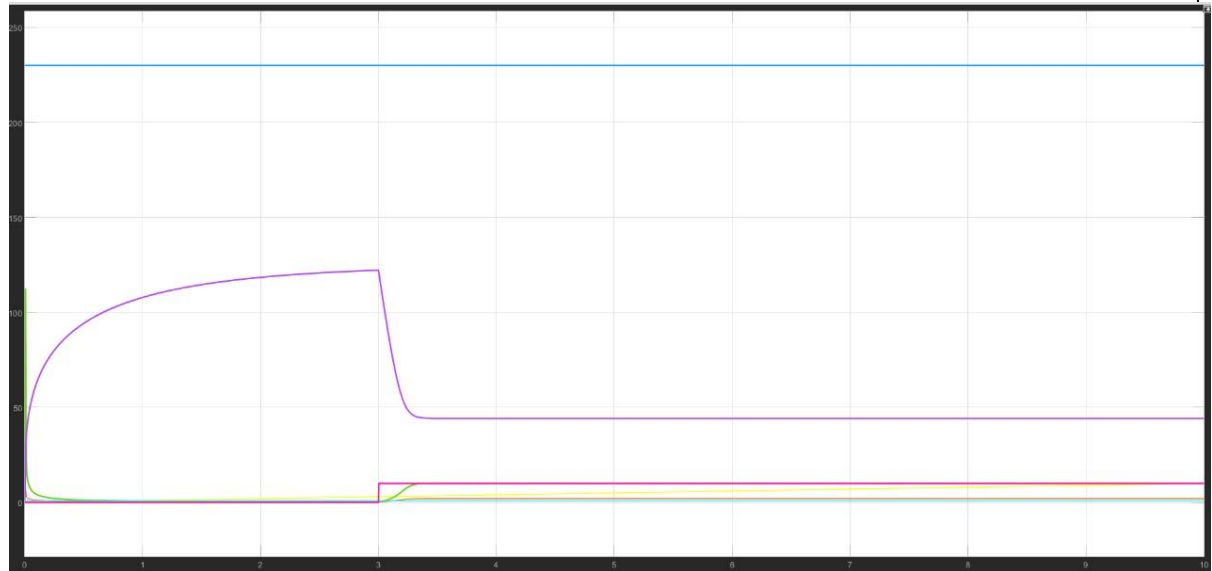

Comparison (Observations)

Parameters	Theoretical Value	Simulation Value
$I_a(A)$	1.99	1.98
$T_e(Nm)$	10.11	10.01
$W_r(rad/sec)$	44.2	44.23

Conclusion:

Experiment performed successfully and theoretical values match the simulation values.

Inference

The dynamic model of a long shunt dc compound motor gives the variation of:

- Armature current
- Speed
- Electromagnetic torque with respect to time.

The variation of these parameters under 2 conditions, i.e no load condition and loaded condition is obtained from the scope.

Initially, these parameters vary rapidly, but with time they attain a constant steady state value.

References: NIL